

Audio Amplifier


Aim


to design and implement a simple audio amplifier circuit capable of amplifying audio signal

Components used

- (i) LM 386 IC
- (ii) Capacitors ($220\mu\text{F}$, $100\mu\text{F}$, $10\mu\text{F}$, 4.7nF , 104)
- (iii) Resistors (10Ω)
- (iv) B-10 k potentiometer
- (v) Audio jack
- (vi) Speaker

• Circuit Diagram

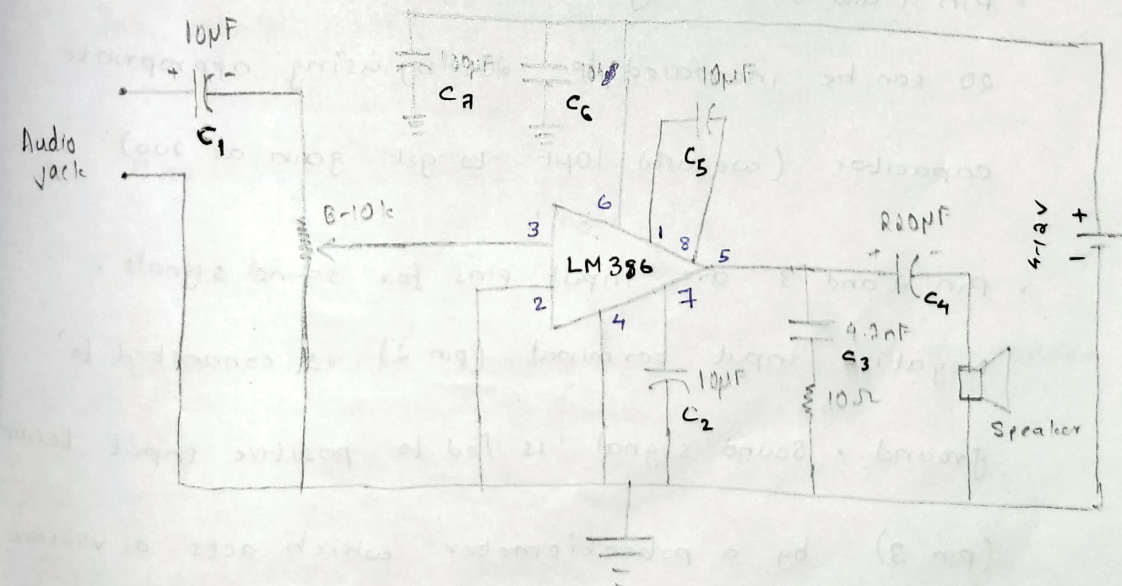

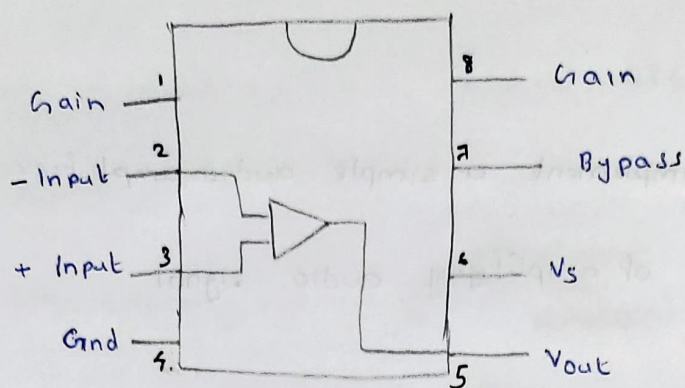

LM386 pin diagram

• Functions of various components (Theory)

(i) LM386

It is a low voltage audio amplifier used in music devices like radio, guitar etc.

- Its gain range is 20-200

- It has wide supply voltage range of 4-12V

Pins:

- Pin 1 and 8 are gain control pins. The default gain 20 can be increased to 200 by using appropriate capacitor (we used 10 μ F to get gain as 200)

- Pin 2 and 3 are input pins for sound signals.

Negative input terminal (pin 2) is connected to

ground. Sound signal is fed to positive input terminal

(pin 3) by a potentiometer which acts as volume control knob.

- Pin 4 and 6 are power supply pins, where pin 4 is connected to ground while pin 6 is connected to $+V_{cc}$.
- Pin 5 is the output pin from which we get the amplified sound signal.
- Pin 7 is a bypass terminal which is grounded using a capacitor for stability.

(ii) Capacitor C_1

It is used to remove the DC component of input signal allowing only AC component to be fed into LM386.

(iii) Capacitor C_2

It is connected to bypass terminal of the IC for stability of circuit.

(iv) Capacitor C_3 and Resistor (10Ω)

They collectively act as a filter circuit called 'Zobel network' used to remove sudden high frequency oscillations/noise.

(v) Capacitor C_4

It is used to remove DC component of output

signal allowing only AC component to be fed into speaker.

(vi) Capacitor C_5

It is used to adjust the gain to its max value.

(vii) Capacitors C_6 and C_7

They're used to reduce the noise of output sound.

(viii) Potentiometer

Act as volume control knob by adjusting the resistance.

• Procedure

- Connect the circuit in circuit diagram on a breadboard
- Connect source voltage between pin 6 ^{or IC} and ground of the circuit.
- Connect audio jack to mobile phone / laptop.

• Observation

- Amplified music/sound is obtained from the speaker.
- On adjusting the value of potentiometer, the loudness and noise from speaker can be adjusted.

• Conclusion

The designed audio amplifier effectively amplifies the given audio signals. It achieves desired amplification with adjustable volume control.

This project demonstrate basic yet effective approach to audio amplification.

• Precaution

- Make sure all the components are connected properly, especially polarised capacitors.
- Make sure that the input voltage is in the specified range (4-12V)